Mark Bellingham - 140320986G4Z1002 CSF Assignment

Truth table for 4 inputs and 7 outputs. The output values in the bottom 6 rows (decimal input values 10 - 15) are marked 'd' because it does not matter what the output is for these inputs.

Z	у	Х	W	а	b	С	d	е	f	g
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1
1	0	1	0	d	d	d	d	d	d	d
1	0	1	1	d	d	d	d	d	d	d
1	1	0	0	d	d	d	d	d	d	d
1	1	0	1	d	d	d	d	d	d	d
1	1	1	0	d	d	d	d	d	d	d
1	1	1	1	d	d	d	d	d	d	d

Karnaugh maps for each of the outputs:

а	XW					
		0 0	0 1	1 1	1 0	
Z	0	1		T	1	
z y	0					
	0 1		1	1	1	
	0 0 0 1 1	d	d	d	d	
b	xw					
		0 0	xw 0 1	1 1	1 0 1	
_		0	1		0	
z y	0	1	1	1	L	
у	0 0 0 1 1	1		1		
	1	d	d	d	đ	
C	xw					
		0 0	0 1	1	1 0	
z y	0	1	1	1		
,	0	1	1	1	1	
	0 0 0 1 1 1	d	d	ď	d	
	1	1	1	d	d	
d			1 xw			
		0 0	0 1	1 1 1	1 0	
z y	0	1		1	1	
,	0				1	
	0 0 0 1 1 1 1	d	d	d	d	
	1	1	1	d	d	

$$a = x + z + y \cdot w + \overline{w} \cdot \overline{y}$$

$$b = \overline{z} \cdot \overline{y} + \overline{x} \cdot \overline{w} + z + x \cdot w$$

$$c = \overline{x} + w + y$$

$$d = z + x \cdot \overline{w} + \overline{z} \cdot \overline{y} \cdot x + \overline{y} \cdot \overline{w} + \overline{x} \cdot w \cdot y$$

е	XW					
		0 0	0	1 1	1 0	
z y	0 0	1			1	
	0				1	
	0 0 0 1 1 1	d	d	d	d	
f	xw					
		0 0	0	1 1	1 0	
z y	0	1				
	0 0 0 1 1		1		1	
	1	d	d	d	d	
g	XW					
		0	0	1 1 1	1 0	
z y	0			1	1	
	0	T	T		1	
	0 0 1 1 1 1 0	d	d	d	đ	
	1 0	1	1	d	d	

$$e = \overline{y} . \overline{w} + z . \overline{x} . \overline{w} + x . \overline{w}$$

$$f = z + \overline{x} \cdot \overline{w} + y \cdot \overline{w} + \overline{x} \cdot y$$

$$g = z + \overline{x} \cdot y + \overline{z} \cdot \overline{y} \cdot x + x \cdot \overline{w}$$

AND gates which are repeated and can therefore be reused in the circuit:

\overline{w} . \overline{y}	$X.\overline{W}$	\overline{z} . \overline{y} . x	\overline{x} . y
a, d, e	d, e, g	d, g	f, g

Screen-prints of the circuit showing each of the 10 decimal digits on the 7-segment display for the relevant binary input.













